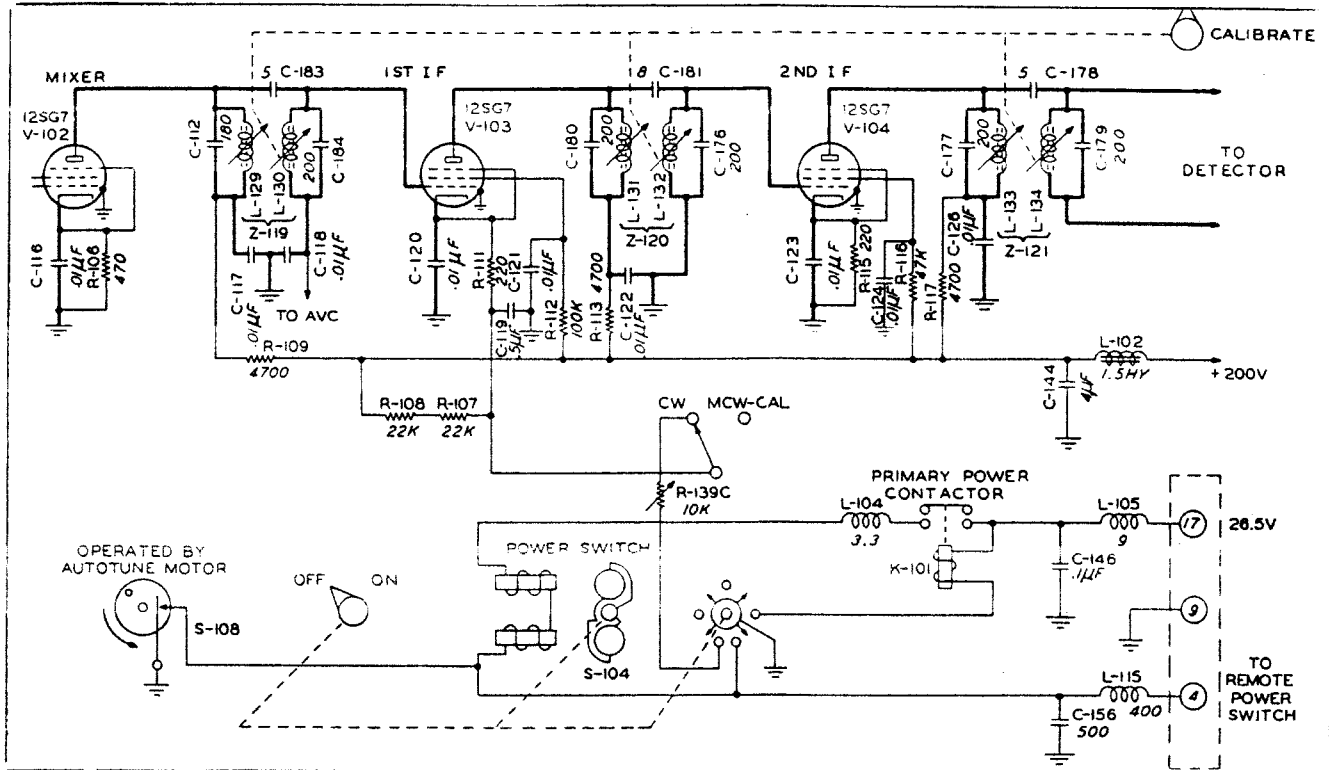




NOTE: Unless otherwise indicated, all resistance values are in ohms, capacitance values are in micromicrofarads, and inductance values are in microhenries.

Figure 4-7. IF Amplifier Circuits




ARR-15 IFT coupling capacitor analysis.
Formula from RDH4, pg 418, Figure 9.12

$$BW / f_o = k = C_m / (C_1 \times C_2) \wedge 0.5$$

	Mixer	1st IF	2nd IF
$C_m =$	5 pF	8 pF	5 pF
$C_1 =$	180 pF	200 pF	200 pF
$C_2 =$	200 pF	200 pF	200 pF
$k =$	0.026	0.042	0.025
$BW =$	13kc	21kc	12.5kc

$$IF \text{ Band Pass} = (13 \text{ kc} + 21 \text{ kc} + 12.5 \text{ kc}) / 3 + 15.5 \text{ kc}$$

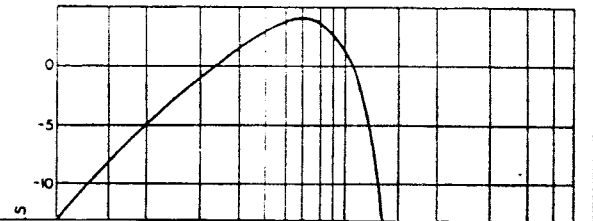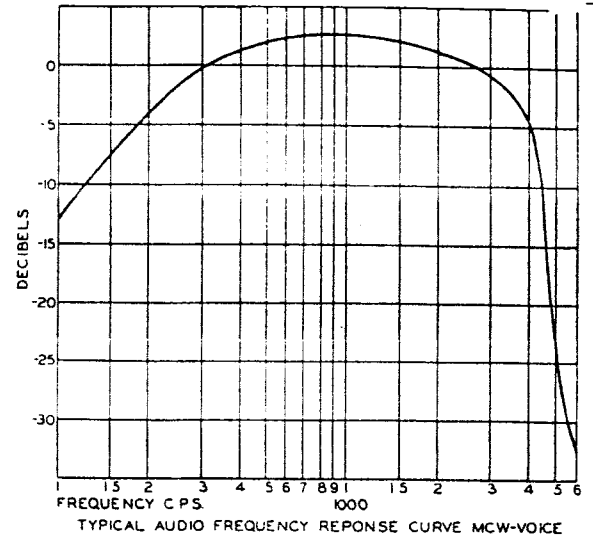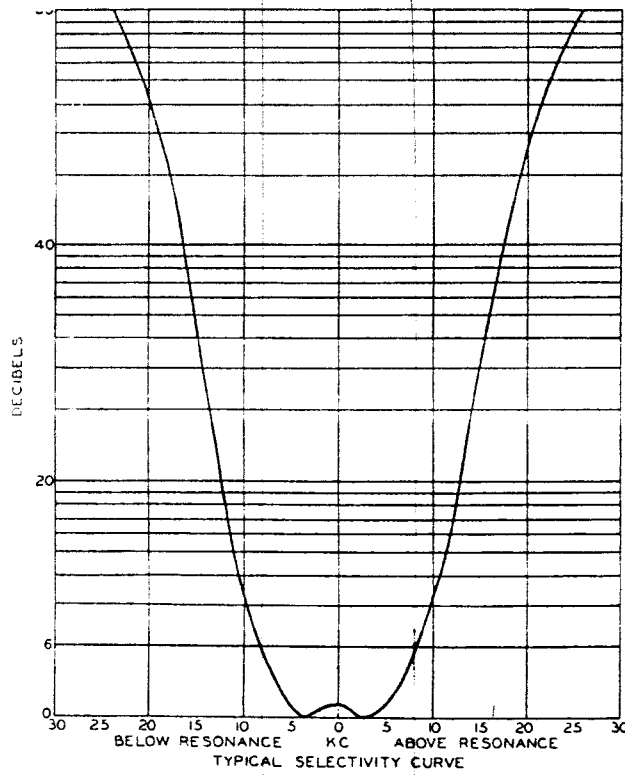From selectivity graph in AN 16-30ARR15-3 on page 5-30
IF Band Pass = approximately 16 kc



Substitute IFT coupling capacitor analysis.

	Mixer	1st IF	2nd IF
Cm =	3 pF	3 pF	3 pF
C1 =	180 pF	200 pF	200 pF
C2 =	200 pF	200 pF	200 pF
k =	0.0016	0.015	0.015
BW =	7.9 kc	7.5 kc	7.5 kc
Total IF Band Pass	= 7.63 kc		
Cm =	3 pF	5 pF	3 pF
C1 =	180 pF	200 pF	200 pF
C2 =	200 pF	200 pF	200 pF
k =	0.0158	0.025	0.015
BW =	7.9 kc	12.5 kc	7.5 kc
Total IF Band Pass	= 9.3 kc		
Cm =	5+6 pF	8+6 pF	5+6 pF
C1 =	180 pF	200 pF	200 pF
C2 =	200 pF	200 pF	200 pF
k =	0.0144	0.0171	0.0137
BW =	7.2 kc	8.55 kc	6.85 kc
Total IF Band Pass	= 7.53 kc		
Cm =	5+3 pF	8+6 pF	5+3 pF
C1 =	180 pF	200 pF	200 pF
C2 =	200 pF	200 pF	200 pF
k =	0.0096	0.0171	0.0094
BW =	4.8 kc	8.55 kc	4.69 kc
Total IF Band Pass	= 6.01 kc		
Cm =	5+5 pF	8+8 pF	5+5 pF
C1 =	180 pF	200 pF	200 pF
C2 =	200 pF	200 pF	200 pF
k =	0.0132	0.02	0.015
BW =	6.6 kc	10 kc	6.25 kc
Total IF Band Pass	= 7.62 kc		