



### K3 - 2S1 INTERFACE CIRCUIT

K3 IS INHIBITED BY SWITCHING ACC-7 BETWEEN 0 AND 5VDC. YOU CAN SELECT WHETHER IS "INHIBIT" OR "ALLOW" BY CHANGING THE K3 MENU SETTING "TX INH". THE CORRECT SETTING FOR THE ABOVE CIRCUIT IS "LO = INH".

----- End of forwarded message -----

for details & usage of various groups is subject to:  
 <> Your use of Yahoo! Groups is subject to:

mailto:groups@yaho.com

N3LD  
 2/9/10